

# Power Electronics for Actuators

# Power Electronics

- Power Electronics drive all mechatronics devices – **Actuators**
- **Power Electronics devices are**
- **Diodes and**
- **Transistors**
- **that can carry large currents and**
- **sustain large voltages**

# Electronics

- Classical / Standard Electronics
  - Electrical quantities carry information
  - Issues: Noise, BER (Bit Error Rate)...
- Power electronics
  - Electrical quantities carry power
  - Issue: Efficiency

# Power Electronics

- Electric power
  - Conversion
  - Control and Applications
  - Conditioning
- Power range:
  - From few **mW** ( $10^{-3}$ ) to few 100s of **MW** ( $10^6$ ,  $10^8$ )


# Power Electronics

1. Power diodes
2. Thyristors
3. Power Bipolar junction transistors (BJT)
4. Insulated-gate bipolar transistors (IGBT)
5. Static Induction Transistors (SIT)


# Power Electronics Devices



Diode

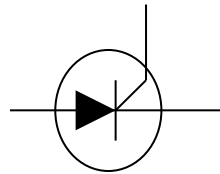

Thyristor

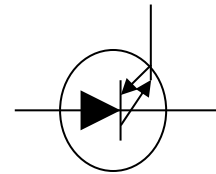

Gate Turnoff  
Thyristor (GTO)




Triac



npn BJT





IGBT

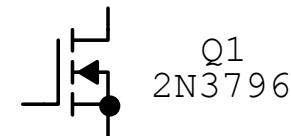

n-channel MOSFET

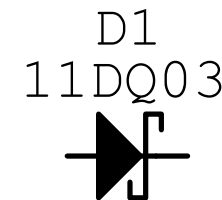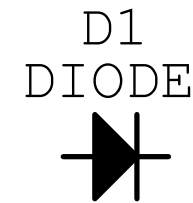
# Power Diodes

- General purpose
  - **3000V, 3500A**
- High-speed (fast-recovery)
  - **3000V, 1000A**
  - Switching time in  **$10^{-6}$  sec ( $\mu$ s)**
- Schottkey
  - **100V, 300A**
  - Switching time in  **$10^{-9}$  sec (ns)**
- $V_D = 0.5$  to  $1.2V$ , can be neglected comparing to 300V


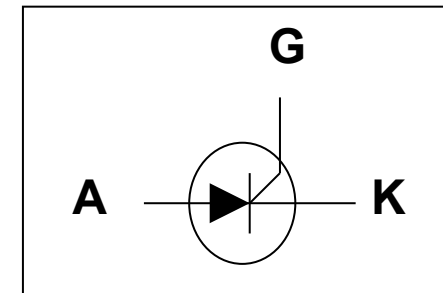
# Thyristors



- **6000V and 3500A**
- Similar to power diodes, but with control
- Gate controls conducting start time
- Starts conducting when
  - gate current  $> 0$ , and  $V_{AK} > 0$
  - Forward  $V_{DROP} = 0.5$  to  $2V$
  - When conducting starts gate current has no control
- Conducting stops with reverse biasing,  $V_{AK} \leq 0$




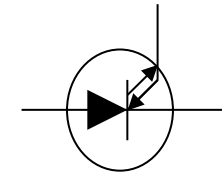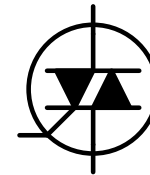
# Thyristors

- There are many different types
- Two most popular are:
  - Triac,
    - Control current in either direction
  - GTO, Gate turnoff thyristor
    - Turned ON by a short positive pulse
    - Can be turned OFF by a short negative pulse



# Power BJTs

- Operate like conventional BJTs, but
- Range **1200V, 400A**
- **Used in power converter applications**
- **Frequency up to 10kHz**

# Power MOSFETs

- Range **1000V, 50A**
- **Frequency up to few 10kHz**


# Power Electronic Circuits

- Voltage regulators
- Power amplifiers
- Switches
- Diode rectifier
- **Power conversion**


# Power Conversion

- AC  $\rightarrow$  DC      Converters – Rectification
- DC  $\rightarrow$  AC      Inversion
- DC  $\rightarrow$  DC      Chopping
- AC  $\rightarrow$  AC      AC voltage controller


# Diode as a Rectifier of AC current

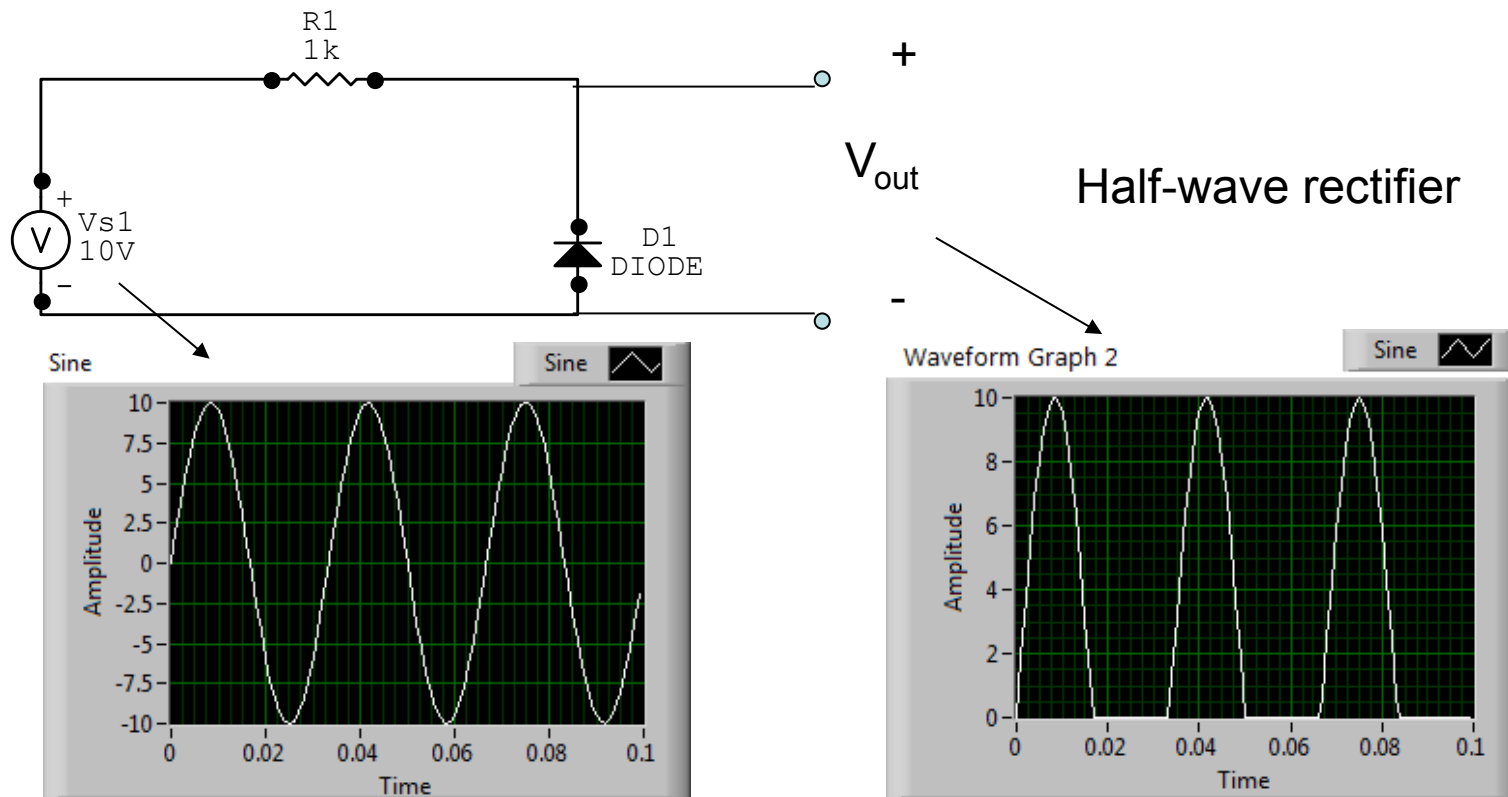

# Full-Wave Bridge Rectifier

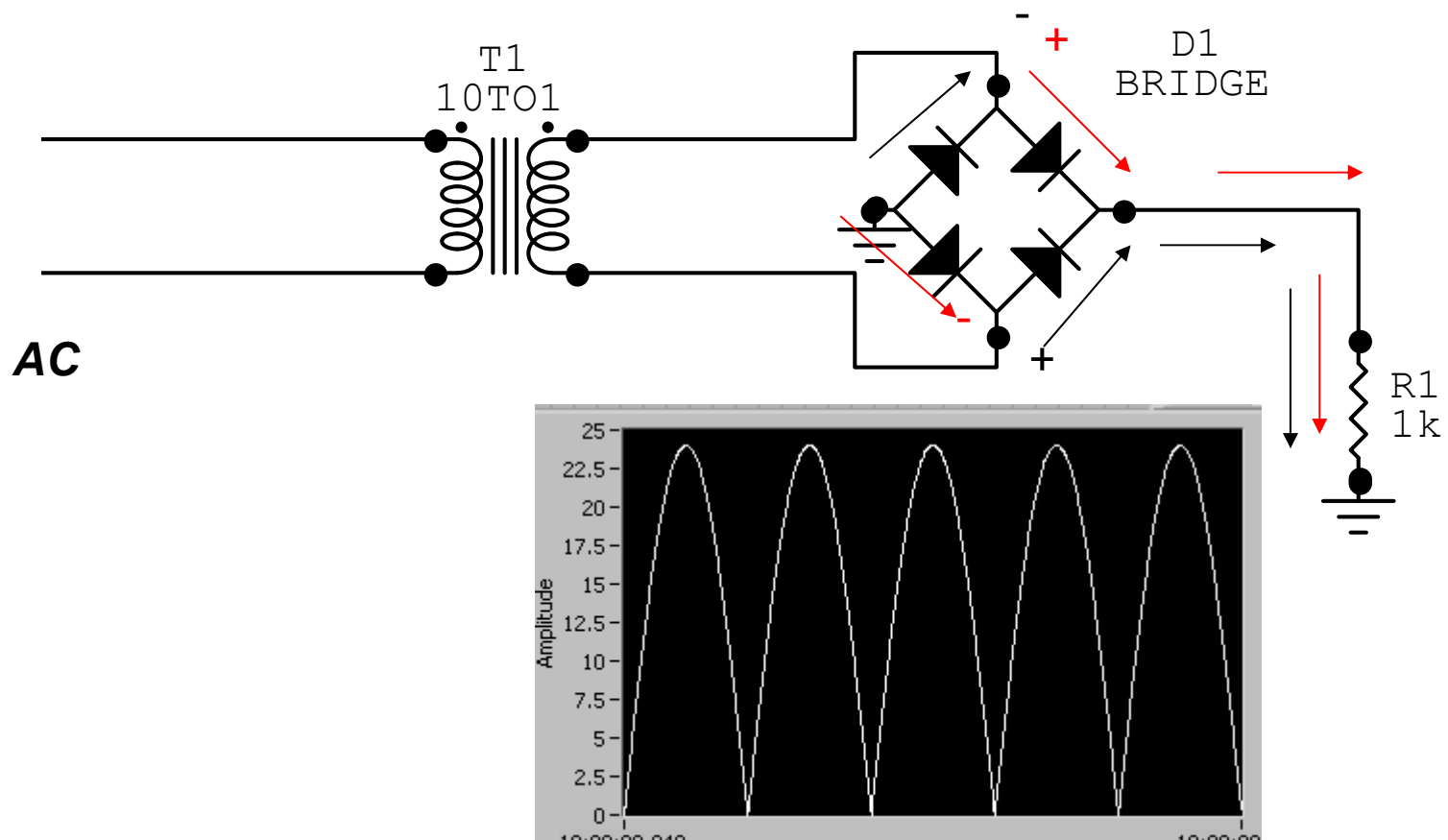

# DC Filtering

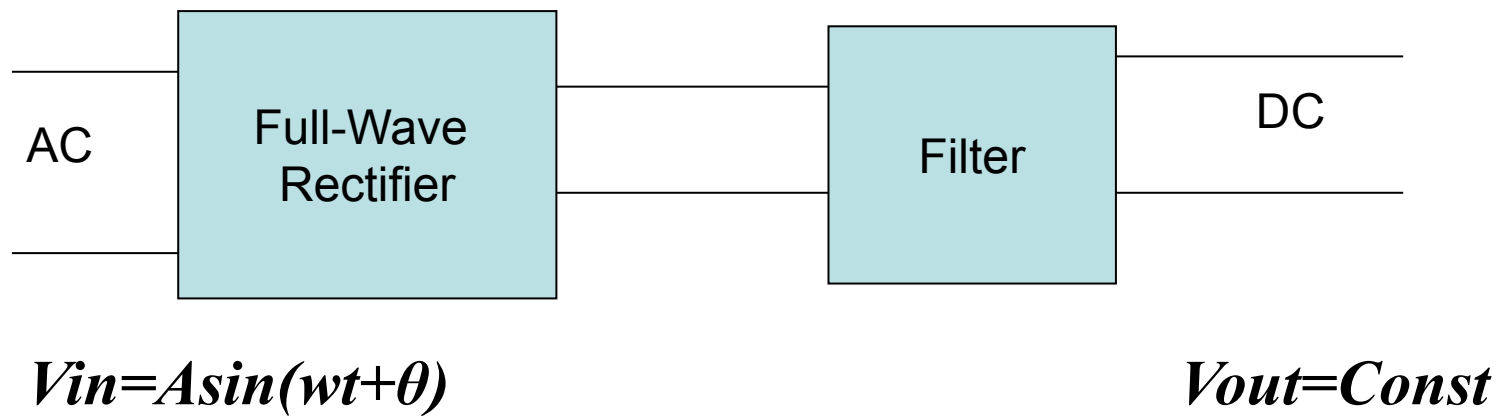



# AC DC Converter With Thyristor


Thyristor can open at any time

$t=[0-T/2]\&[T/2-T]$


Variable DC output

Used for DC motors power supply

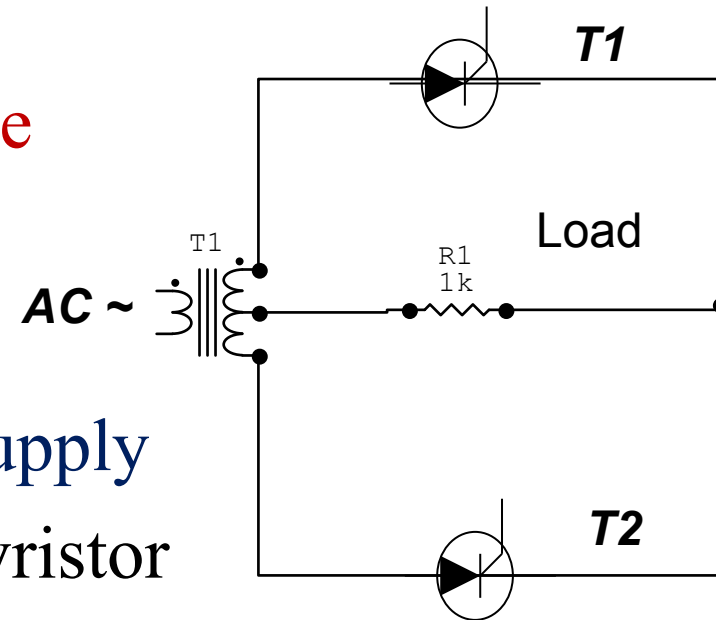Angle  $\alpha$  is firing angle of Thyristor



$\alpha$

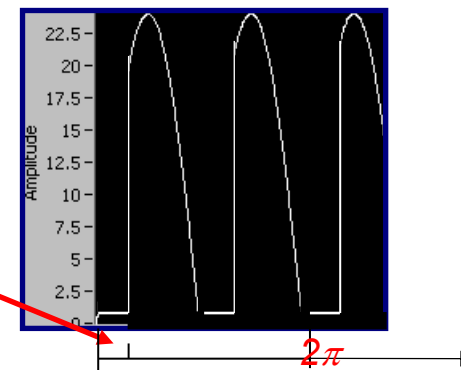

# AC DC Converter With Thyristor

$$v_s(\omega t) = 0, \quad 0 \leq \omega t \leq \alpha$$

$$v_s(\omega t) = V_m \sin(\omega t) \quad \alpha \leq \omega t \leq \pi$$

$$v_s(\omega t) = 0, \quad \pi \leq \omega t \leq \pi + \alpha$$

$$v_s(\omega t) = -V_m \sin(\omega t) \quad \pi + \alpha \leq \omega t \leq 2\pi$$

# Calculate Average Voltage, RMS


- RMS

$$V_{RMS}^2 = \frac{1}{T} \int_0^T v^2 dt$$


- Average value

$$V_{av} = \frac{1}{T} \int_0^T v dt$$


# AC AC Converter

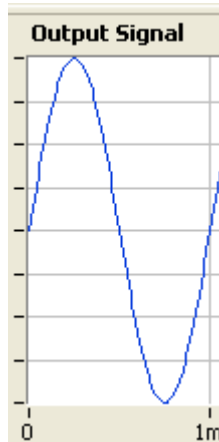

$$v = V_m \sin(\omega t)$$

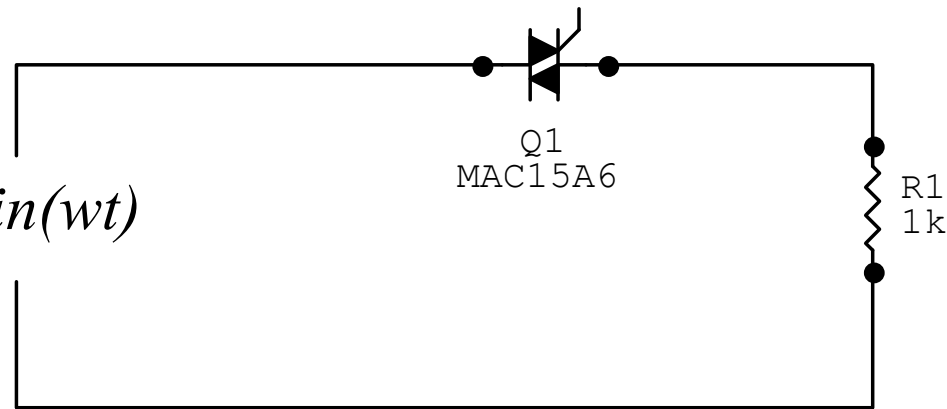

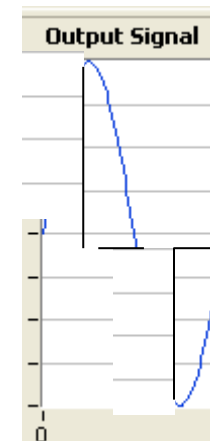Variable AC from fixed AC  
 Resulting AC is not pure sinusoid  
 Bidirectional control of RMS



*Alternating Current (AC) Harmonic Waveform* => *Alternating Current (AC) Non-harmonic Waveform*

# AC AC Converter with Triac

$$v_s(\omega t) = 0, \quad 0 \leq \omega t \leq \alpha$$

$$v_s(\omega t) = V_m \sin(\omega t) \quad \alpha \leq \omega t \leq \pi$$


$$v_s(\omega t) = 0, \quad \pi \leq \omega t \leq \pi + \alpha$$

$$v_s(\omega t) = V_m \sin(\omega t) \quad \pi + \alpha \leq \omega t \leq 2\pi$$

# DC DC Converter

- Known as **Chopper**, or **Switching regulator**
- Converts fixed DC source voltage to a variable DC supply, i.e.
- Converts DC source to a variable-duty-cycle output voltage
- Application: **Run DC electric motors used in electric vehicles**

# DC DC Converter

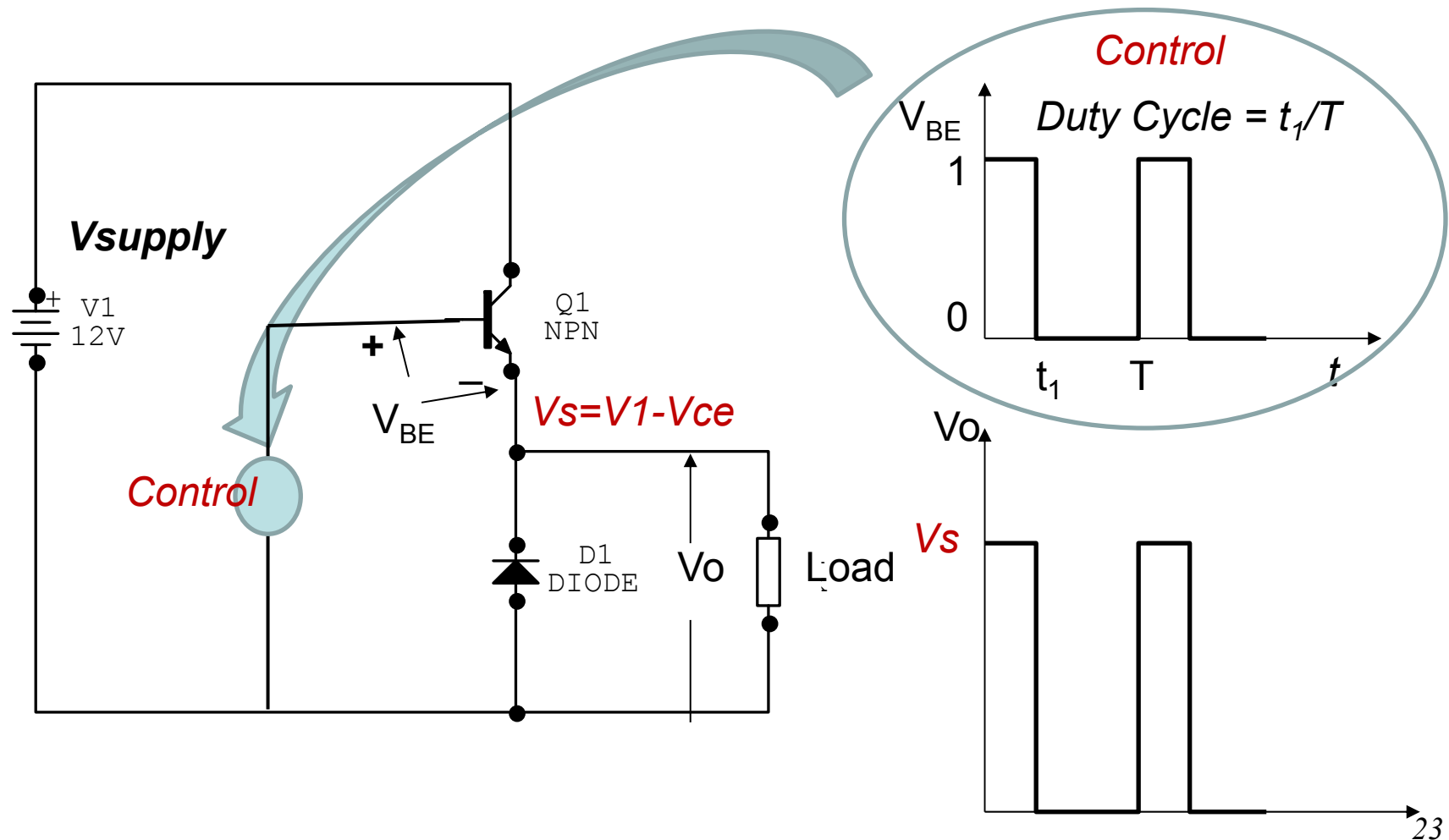


# DC to AC, Inversion


- Battery 12V to 240, 50Hz
- Solar panels
- Fuel cells
  
- Applications: AC motor control



# Inverter With Electromechanical Switch

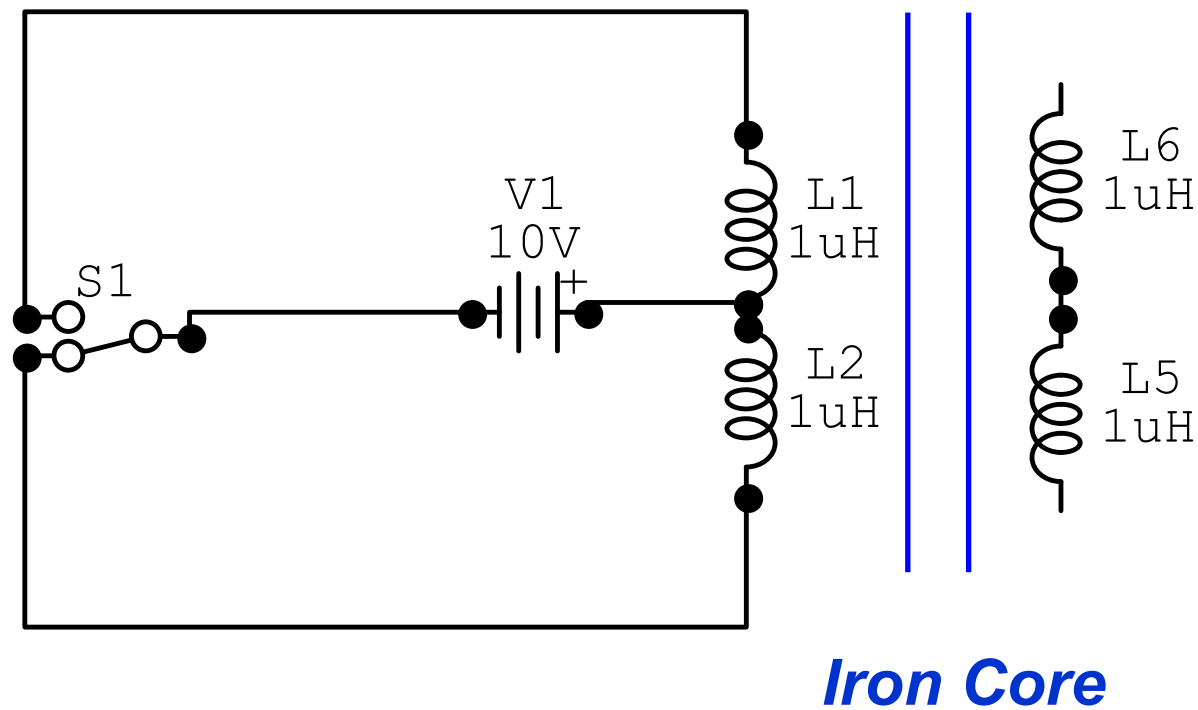

# Inverter With an Electronic Switch

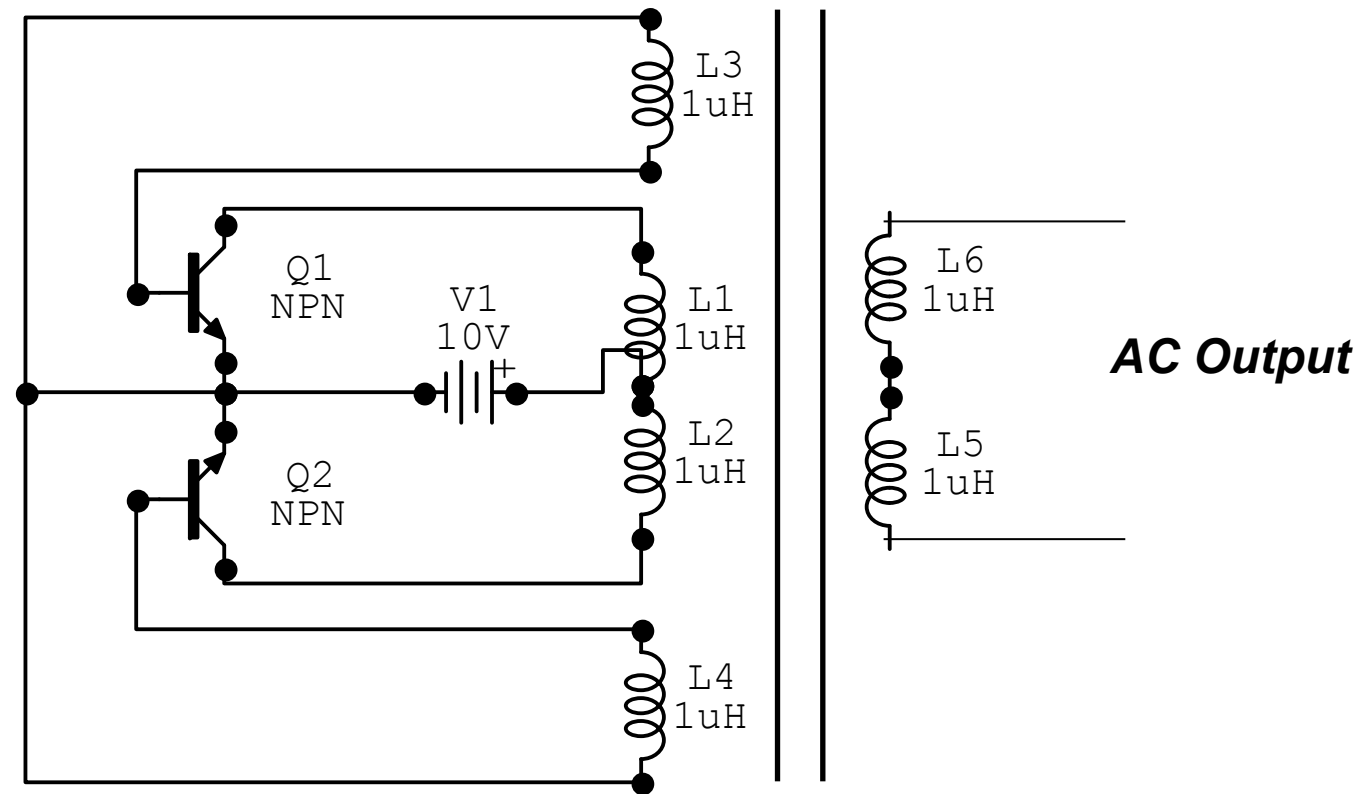

# Basic Revision 1

Ohm's law:

Kirchhoff's current law:

Kirchhoff's voltage law:


# Basic Revision 1

Ohm's law:  $V=R*I$

# Basic Revision 1

Kirchhoff's current law:

$$\sum_{k=1}^n I_k = 0$$

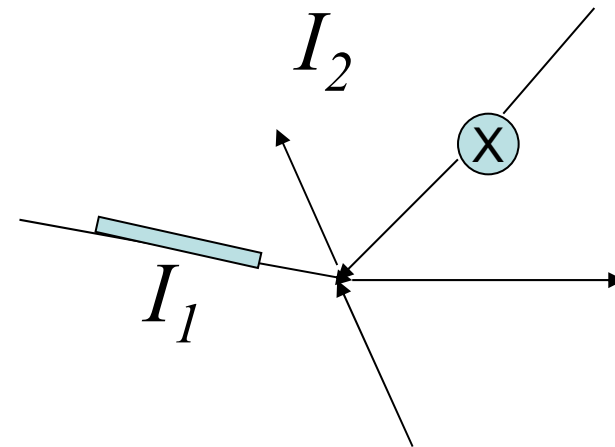


# Basic Revision 1

Kirchhoff's voltage law:


$$\sum_{k=1}^n V_k = 0$$

$$E = V_1$$

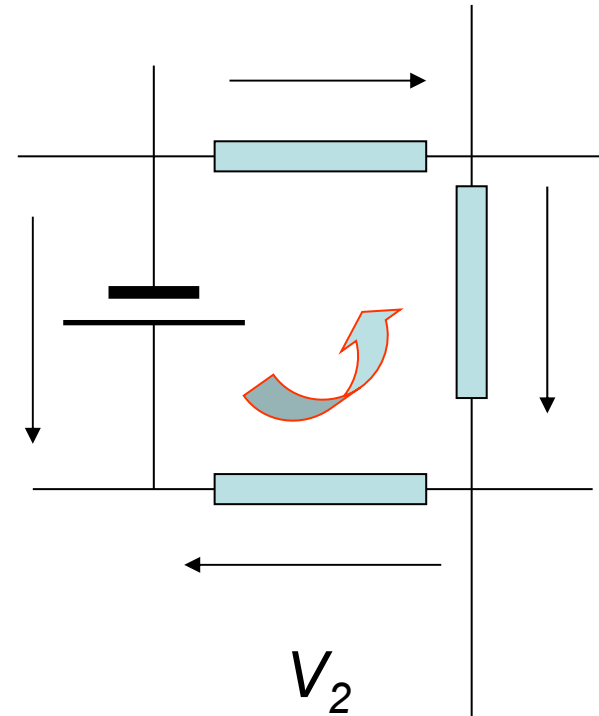

# Basic Revision 1

Ohm's law:

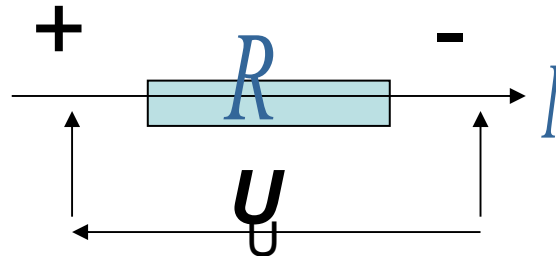

$$\text{Voltage} = \text{Resistance} * \text{Current}$$


*Across Variable = Proportional Element \* Through Variable*

*Find the voltage if  $I=14mA$  and  $R=1k\Omega$*

*Our resistance is = ?*

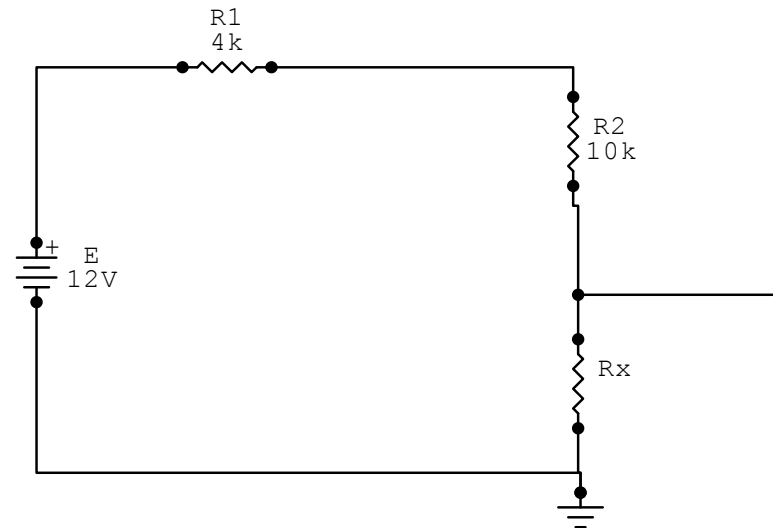
## Basic Revision 2

- What is the value of the resistance  $R_x$ , as shown in the Figure 3, if the output voltage is 5V?
- *What is the amount of Power dissipation on the resistor  $R_1$ ,  $R_2$ ,  $R_x$  ?*





# Question 1

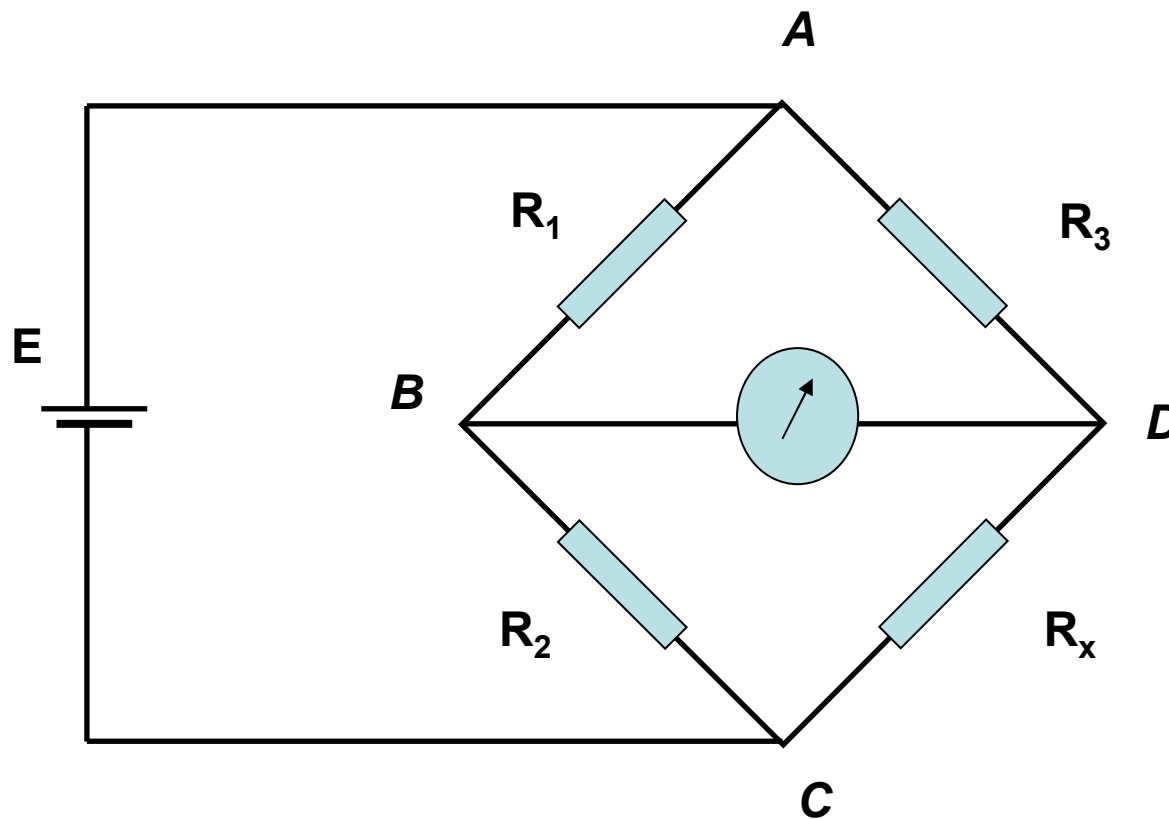

$$E=12V$$

$$R_1=2k$$

$$R_2=4k$$

$$R_3=0.5k$$

Find

$$R_x=?,$$

so that

$$I_{BD}=0$$

How do we call this circuit?

Where is it used?

## Question 2


Calculate an AC Circuit Impedance:

$$Z=? \quad R=200\Omega, L=1mH, C=1nF$$


$$Z = R + j\omega L - j\frac{1}{\omega C}$$

$$Z = R + j2\pi fL - j\frac{1}{2\pi fC}$$
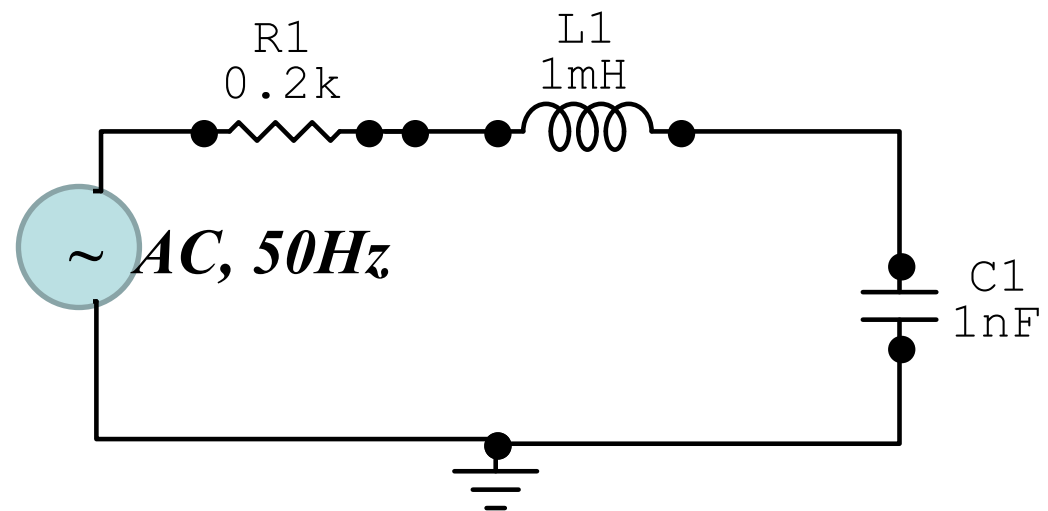
$$Z = R + j\left(2\pi fL - \frac{1}{2\pi fC}\right)$$



## Question 3

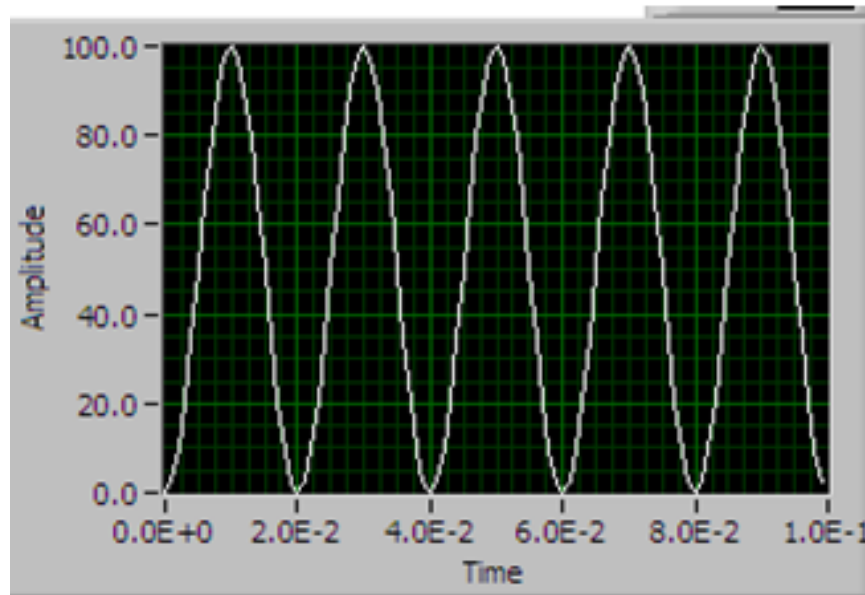

- What are the period and the frequency of the signal waveform?
  - What is the average value of the voltage?
  - What is RMS value of the voltage waveform?
- Amplitude is shown in [V].

1. Write an analytical expression for the shown waveform.

Thank you,  
Questions

