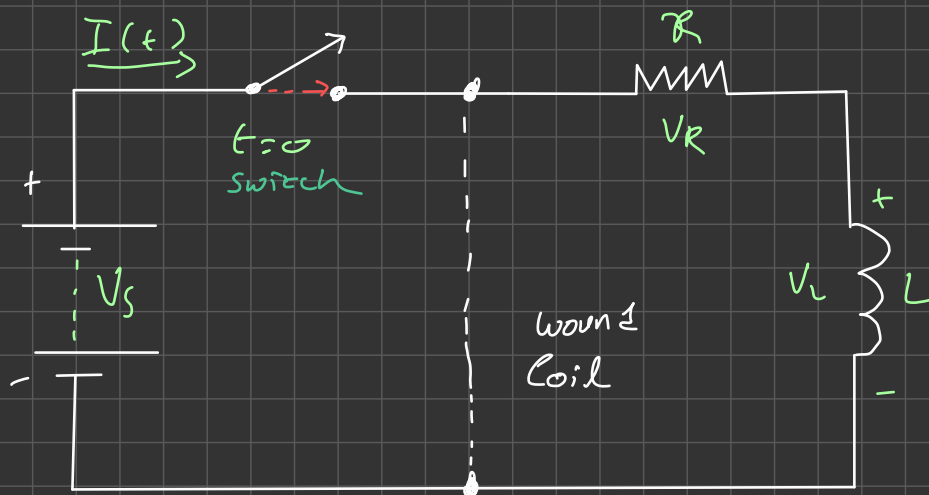


DC Modelling





When electromotive force (emf) is removed from a circuit containing inductance and resistance but no capacitors, and rate of decrease of current is proportional to the current.

If the initial current is 30 A but decays to 11 A after 0.01 seconds find an expression for the current

Rate of decrease of current $\frac{dI}{dt} = -RI$

where R is the constant of proportionality.

$$\Rightarrow \frac{dI}{dt} = -RI$$

$$\Rightarrow \frac{dI}{I} = -R dt \Rightarrow \int \frac{dI}{I} = \int -R dt \Rightarrow \ln |I| = -Rt + C$$

$$\Rightarrow \ln |I| = -Rt + C$$

$$\Rightarrow \log_e I = -Rt + C$$

$$\Rightarrow e^{(\log_e I)} = e^{(-Rt + C)}$$

$$\Rightarrow \therefore I(t) = e^{-Rt + C}$$

Since at $t = 0$, $I(0) = 30$ A

$$\therefore I(0) = 30 = e^{-0 + C}$$

$$\Rightarrow 30 = e^C \Rightarrow e^C = 30$$

$$\therefore I(t) = e^{-Rt} e^C = e^{-Rt} (30)$$

$$\therefore I(t) = 30e^{-Rt}$$

Since $I(t) = 30 e^{-\mathcal{R}t}$

and $I(0.01) = 11 \text{ A}$


$\therefore I(t) = 30 e^{-\mathcal{R}t}$

$$\begin{aligned} \ln |I(t)| &= \ln |30 e^{-\mathcal{R}t}| \\ &= \ln |30| + \ln |e^{-\mathcal{R}t}| \\ &= \ln |30| - \mathcal{R}t \end{aligned}$$

$\therefore \mathcal{R}t = \ln |30| - \ln |I(t)|$

$$\therefore \mathcal{R} = \frac{\ln \left| \frac{30}{I(t)} \right|}{t} = \frac{\ln \left| \frac{30}{11} \right|}{0.01} = 100 \cdot 3302$$

$\therefore I(t) = 30 e^{-100.3302 t}$

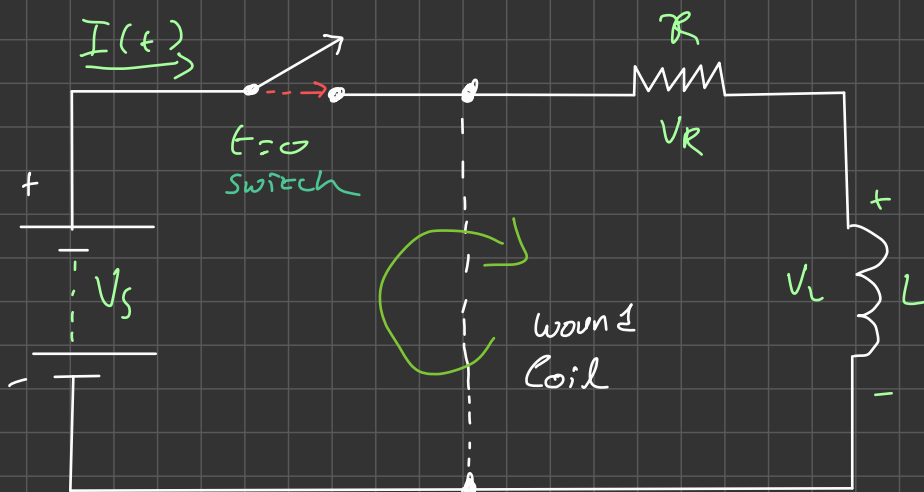

LR series circuit is connected constant voltage source (battery) and a switch.

Assume that the switch, S , is open until it is closed at a time $t=0$, then remains permanently closed producing a "step response" type voltage input.

$$\begin{aligned} \Sigma V=0 &\Rightarrow -V_s + V_R + V_L = 0 \Rightarrow V_s - (V_R + V_L) = 0 \\ &\Rightarrow V_s - \left\{ IR + L \frac{dI}{dt} \right\} = 0 \\ &\Rightarrow V_s - IR - L \frac{dI}{dt} = 0 \\ &\Rightarrow L \frac{dI}{dt} = V_s - IR \end{aligned}$$

$$\begin{aligned} \therefore \frac{dI}{V_s - IR} &= \frac{1}{L} dt \Rightarrow \int \frac{dI}{V_s - IR} = \int \frac{1}{L} dt \\ &\Rightarrow \frac{1}{\frac{d}{dI}(V_s - IR)} \ln |V_s - IR| = \frac{1}{L} t + C \\ &= -\frac{1}{R} \ln |V_s - IR| = \frac{t}{L} + C \end{aligned}$$

Continue...
 \Rightarrow

